


A.C. Power Analysis Example

Problem: In the following circuit, $V_L = 240 \text{ V}_{\text{RMS}}$ at all times.

The loads operate under following conditions

α_1 : absorbs 180 Watts and 240 Vars


α_2 : absorbs 600 VA at 0.6 p.f. lagging

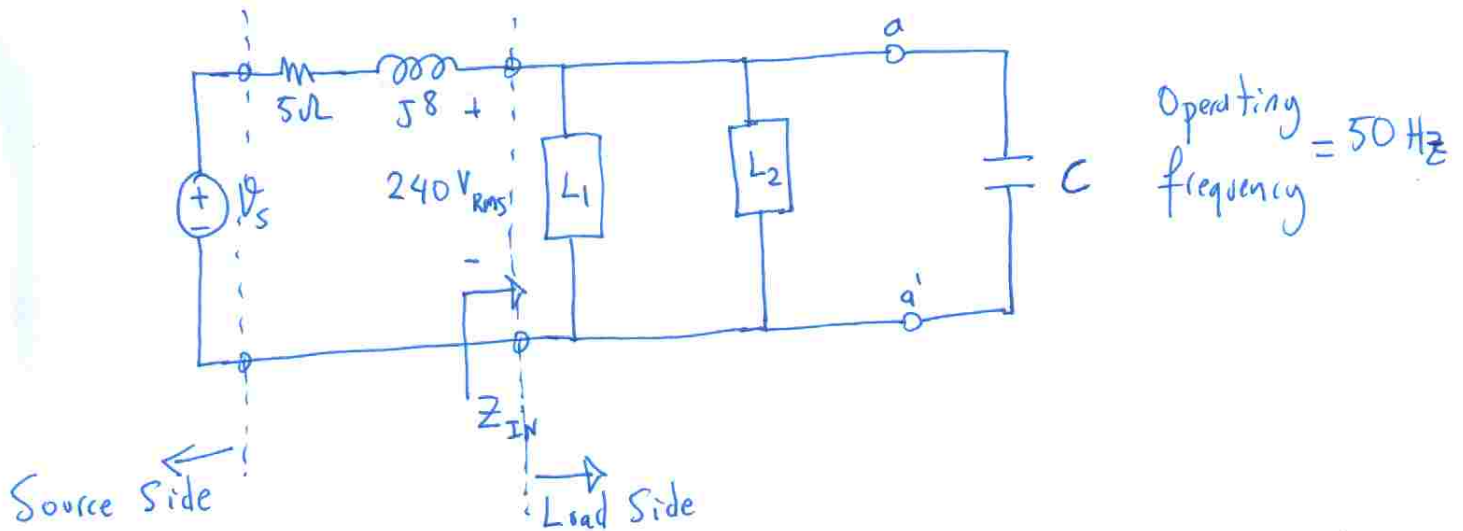

- Assume there is no capacitor between a-a' lines. Find the input impedance at load side, source voltage in RMS, p.f. on the source side and also calculate the efficiency of the system. (Efficiency is the ratio of real power delivered to the load side and real power generated by the source.)
- Now, a capacitor is connected between a-a' terminals. Find C in Farad's such that efficiency is maximized. Find V_s in RMS.
- Find C such that load side p.f. is 0.9 lagging. Find V_s after the connection of the Capacitor.

Solution:

a) No capacitor

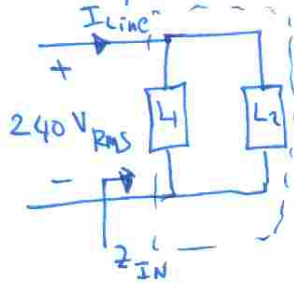

$$S_{L1} = 180 + j240$$

$$S_{L2} = 600 \cos^{-1}(0.6) = 360 + j480$$

$$+ \frac{S_{L1} + S_{L2}}{S_{Total}^{Load} = 540 + j720}$$


I

$$|S_{Total}^{Load}| = V_{Load}^{RMS} \cdot I_{Load}^{RMS} \Rightarrow |540 + j720| = 240 \cdot I_{Line}^{RMS}$$

$$I_{Line}^{RMS} = \frac{900}{240} = 3.75 \text{ A}_{RMS}$$

II
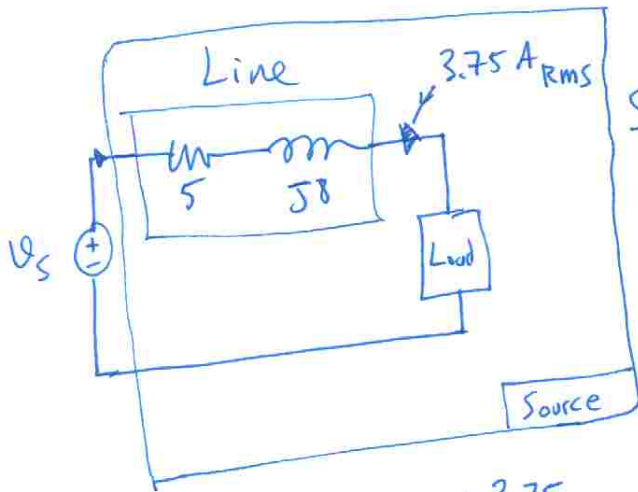
$$S_{Total}^{Load} = (I_{Line}^{RMS})^2 Z_{IN} \rightarrow Z_{IN} = \frac{540 + j720}{(3.75)^2} = 38.4 + j51.2 = 64 \angle 53.1^\circ$$



$$S_{Line} = (I_{Line}^{RMS})^2 \cdot (5 + j8) = 70.3125 + j112.5$$

$$S_{Source} = S_{Line} + S_{Total}^{Load} = 610.3125 + j832.5$$


III

$$|S_{Source}| = V_S^{RMS} \cdot I_{Line}^{RMS} \rightarrow V_S^{RMS} = \frac{1610.3125 + j832.5}{3.75} = 275.26 \text{ V}_{RMS}$$

$$p.f. \text{ on source side} = \cos\left(\tan^{-1} \frac{832.5}{610.3125}\right) = 0.59 \text{ lagging}$$

$$\text{Efficiency} = \frac{P_{delivered} \text{ (watts)}}{P_{generated} \text{ (watts)}} = \frac{540 \text{ (watts)}}{540 + 70.3125 \text{ (watts)}} = 88.48 \%$$

b) With capacitor

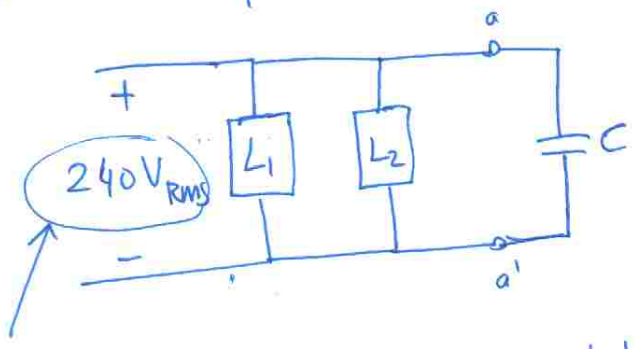

$$\text{Efficiency} = \frac{P_{\text{Load}}}{P_{\text{Load}} + P_{\text{Line}}}$$

Since both loads operate as in part a; that is

$$S_{\text{Total}}^{\text{Load w/Cap}} = 540 + j720$$



To maximize efficiency, we need to minimize line losses.

$$\text{Efficiency} = \frac{540}{540 + P_{\text{Line}}}$$

$$P_{\text{Line}} = (I_{\text{Line}}^{\text{RMS}})^2 R_{\text{Line}} \rightarrow \text{so we need to minimize } I_{\text{Line}}^{\text{RMS}}$$

\uparrow
 5Ω



so we need to change the load side p.f. to unity!!

Before Compensation

$$S_{\text{Loads}}^{\text{Before}} = 540 + j720$$

$$I_{\text{Line}}^{\text{Before}} = 3.75 \text{ A}_{\text{RMS}}$$

After Compensation (Desired)

$$S_{\text{Loads+Cap}}^{\text{After}} = 540 + j720 - j720 = 540 \text{ (unity p.f. is achieved)}$$

$$I_{\text{Line}}^{\text{after}} = \frac{540}{240} = 2.25 \text{ A}$$

$$S_{\text{Line}}^{\text{after}} = (2.25)^2 (5 + j8) = 25.31 + j40.5$$

$$S_{\text{Source}}^{\text{after}} = 540 + 25.31 + j40.5$$

$$S_{\text{Source}}^{\text{after}} = 565.31 + j40.5$$

$$|S_{\text{Source}}^{\text{after}}| = 566.75 = V_{S_{\text{RMS}}}^{\text{after}} \cdot \underbrace{I_{\text{Line}}^{\text{RMS}}}_{2.25}$$

$$V_{S_{\text{RMS}}}^{\text{after}} = 251.89 \text{ V}_{\text{RMS}}$$

$$\text{Efficiency} = \frac{540}{565.31} = 95.5\%$$

$$S_{\text{compensator}} = -j720 = \frac{(V_{\text{cap}}^{\text{RMS}})^2}{X_c^*} \rightarrow X_c^* = \frac{(240)^2}{-j720} = j80$$

$$X_c = -j80$$

$$C = \frac{1}{(2\pi 50) 80} = 39.8 \mu\text{F}$$

$$X_c = \frac{1}{j\omega C} = \frac{1}{j(2\pi 50) C}$$

c) Before

$$S_{\text{Loads}} = 540 + j720$$



After

$$S_{\text{Loads} + \text{cap}} = 540 + j720 + S_{\text{cap}}$$

$$S_{\text{cap}} = -jQ_{\text{cap}}$$

$$= 540 + j(720 - Q_{\text{cap}})$$

$$\text{p.f. (desired)} = 0.9$$

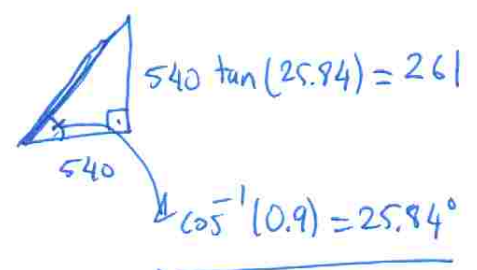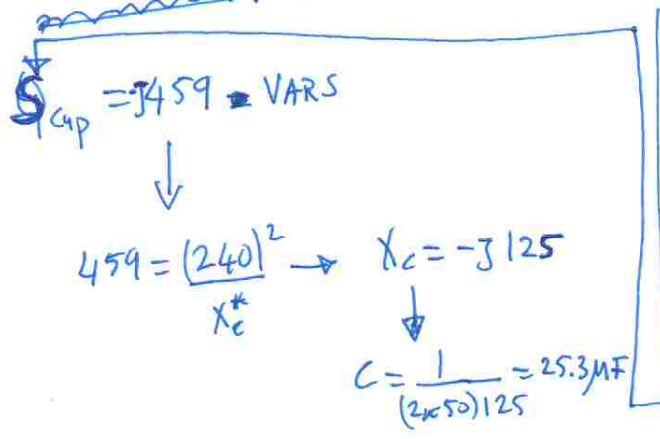

Then $720 - Q_{\text{cap}} = 261 \rightarrow Q_{\text{cap}} = 459$